

# 可编程逻辑阵列


刘鹏

浙江大学信息与电子工程学院

liupeng@zju.edu.cn
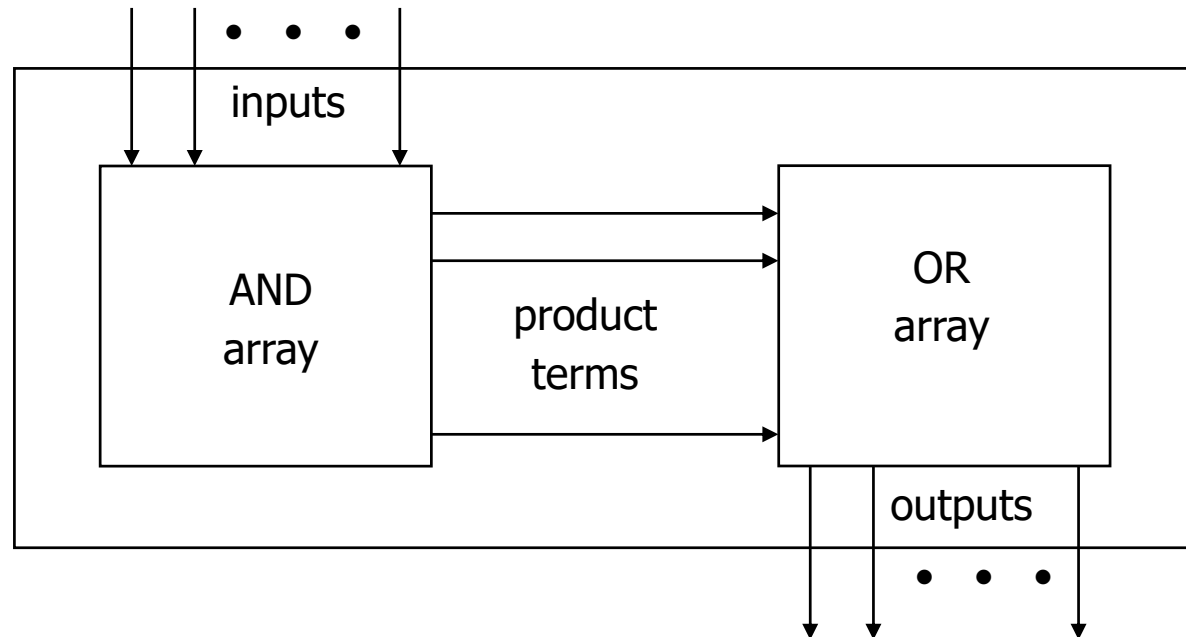
# 可编程逻辑阵列 (Programmable Logic Arrays, PLAs)

- Pre-fabricated building block of many AND/OR gates
  - Actually NOR or NAND
  - "Personalized" by making or breaking connections among gates
  - Programmable array block diagram for sum of products form



# 使能概念 (Enabling Concept)

- Shared product terms among outputs

example:

$$\begin{aligned}F0 &= A + B' C' \\F1 &= A C' + A B \\F2 &= B' C' + A B \\F3 &= B' C + A\end{aligned}$$

personality matrix

product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	—	0	1	1	0
B'C	—	0	1	0	0	0	1
AC'	1	—	0	0	1	0	0
B'C'	—	0	0	1	0	1	0
A	1	—	—	1	0	0	1

input side:

1 = uncomplemented in term  
0 = complemented in term  
— = does not participate


output side:

1 = term connected to output  
0 = no connection to output


reuse of terms
 
# 编程前

- All possible connections available before "programming"
  - In reality, all AND and OR gates are NANDs




# PLD符号

 

 
# 编程后

- Unwanted connections are "blown"
  - Fuse (normally connected, break unwanted ones)
  - Anti-fuse (normally disconnected, make wanted connections)


 
# 高扇入 (Fan-in) 结构的一种表示


- Short-hand notation--don't have to draw all the wires
  - Signifies a connection is present and perpendicular signal is an input to gate



notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

 


# 可编程逻辑阵列例子

## □ Multiple functions of A, B, C

- $F1 = A B C$
- $F2 = A + B + C$
- $F3 = A' B' C'$
- $F4 = A' + B' + C'$
- $F5 = A \text{ xor } B \text{ xor } C$
- $F6 = (A \text{ xnor } B \text{ xnor } C)'$

A	B	C	F1	F2	F3	F4	F5	F6
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	1	1	1
0	1	0	0	1	0	1	1	1
0	1	1	0	1	0	1	0	0
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	0
1	1	0	0	1	0	1	0	0
1	1	1	1	1	0	0	1	1

 



# PLA 设计例子

## □ BCD to Gray code converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	—	—	—	—	—
1	1	—	—	—	—	—	—

minimized functions:

$$W = A + B D + B C$$

$$X = B C'$$

$$Y = B + C$$

$$Z = A'B'C'D + B C D + A D' + B' C D'$$

				A	
0	0	X	1		
0	1	X	1		
0	1	X	X	D	
0	1	X	X		
C					
				B	

K-map for W

				A			
		0	1	X	0		
		0	1	X	0		
C		0	0	X	X	D	
		0	0	X	X		
						B	

K-map for X

A				
0	1	X	0	
0	1	X	0	
C	1	1	X	X
	1	1	X	X
B				
D				


K-map for Y

A			
0	0	X	1
1	0	X	0
0	1	X	X
1	0	X	X
C		D	
B			

K-map for Z

# PLA 设计例子

## □ Code converter: programmed PLA

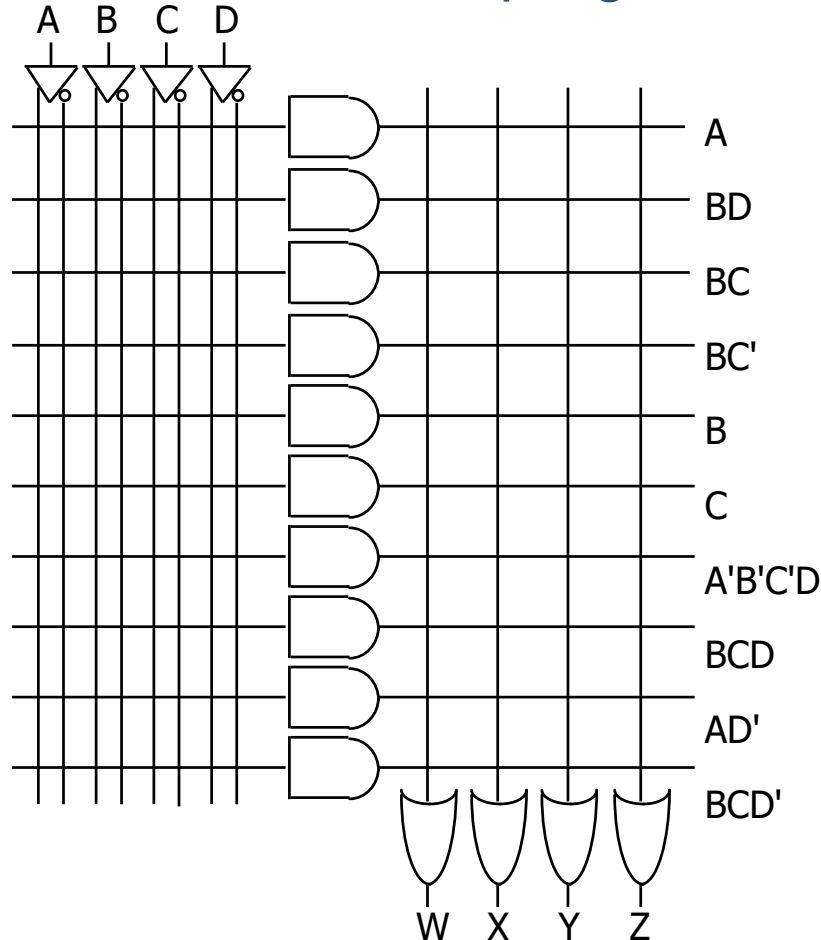

minimized functions:

$$W = A + B D + B C$$

$$X = B C'$$

$$Y = B + C$$

$$Z = A' B' C' D + B C D + A D' + B' C D'$$

not a particularly good  
candidate for PLA  
implementation since no terms  
are shared among outputs

however, much more compact  
and regular implementation  
when compared with discrete  
AND and OR gates

# PLA设计例子

## □ BCD to Gray code converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	—	—	—	—	—
1	1	—	—	—	—	—	—

minimized functions:

W =  
X =  
Y =  
Z =

			A	
	0	0	X	1
	0	1	X	1
C	0	1	X	X
	0	1	X	X
			B	

K-map for W

			A	
	0	1	X	0
	0	1	X	0
C	0	0	X	X
	0	0	X	X
			B	

K-map for X

			A	
	0	1	X	0
	0	1	X	0
C	1	1	X	X
	1	1	X	X
			B	

K-map for Y

			A	
	0	0	X	1
	1	0	X	0
C	0	1	X	X
	1	0	X	X
			B	

K-map for Z


# PLA 设计例子#1

## □ BCD to Gray code converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	—	—	—	—	—
1	1	—	—	—	—	—	—

minimized functions:

W =  
X =  
Y =  
Z =

 

# PLA 设计例子#2

## □ Magnitude comparator

	A				
	1	0	0	0	
	0	1	0	0	D
C	0	0	1	0	
	0	0	0	1	
	B				

K-map for EQ

	A				
	0	1	1	1	
	1	0	1	1	D
C	1	1	0	1	
	1	1	1	0	
	B				


K-map for NE

	A				
	0	0	0	0	
	1	0	0	0	D
C	1	1	0	1	
	1	1	0	0	
	B				

K-map for LT




	A				
	0	1	1	1	
	0	0	1	1	D
C	0	0	0	0	
	0	0	1	0	
	B				

K-map for GT

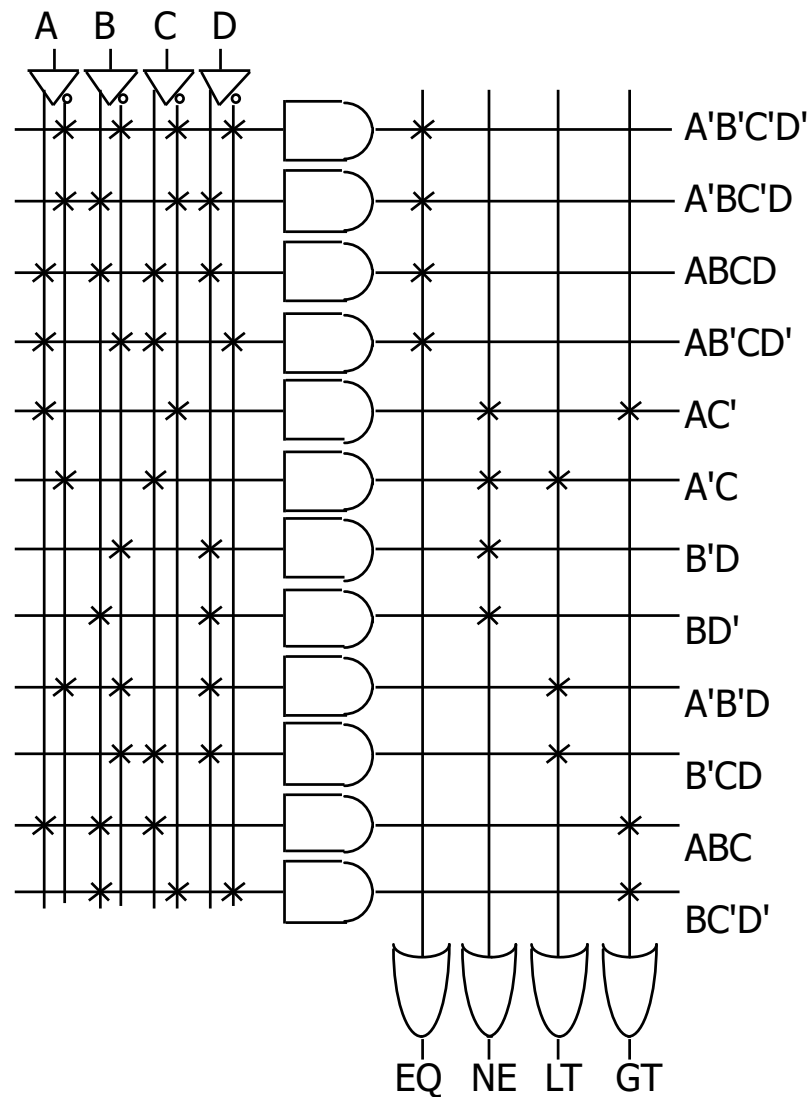
   
# 多路选择器/解复器

- ❑ Direct point-to-point connections between gates
- ❑ *Multiplexer*: route one of many inputs to a single output
- ❑ *Demultiplexer*: route single input to one of many outputs



# 多路选择器

## □ Multiplexers/Selectors: general concept

- $2^n$  data inputs,  $n$  control inputs (called "selects"), 1 output
- Used to connect  $2^n$  points to a single point
- Control signal pattern forms binary index of input connected to output

$$Z = A' I_0 + A I_1$$

functional form

logical form




two alternative forms  
for a 2:1 Mux truth table

A	Z
0	$I_0$
1	$I_1$

$I_1$	$I_0$	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# 多路选择器

   
- 2:1 mux:  $Z = A' I_0 + A I_1$
- 4:1 mux:  $Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$
- 8:1 mux:  $Z = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$
- In general,  $Z = \sum_{k=0}^{2^n-1} (m_k I_k)$ 
  - in minterm shorthand form for a  $2^n:1$  Mux





 
# 多路选择器级联

- ❑ Large multiplexers implemented by cascading smaller ones




control signals B and C simultaneously choose one of I0, I1, I2, I3 and one of I4, I5, I6, I7

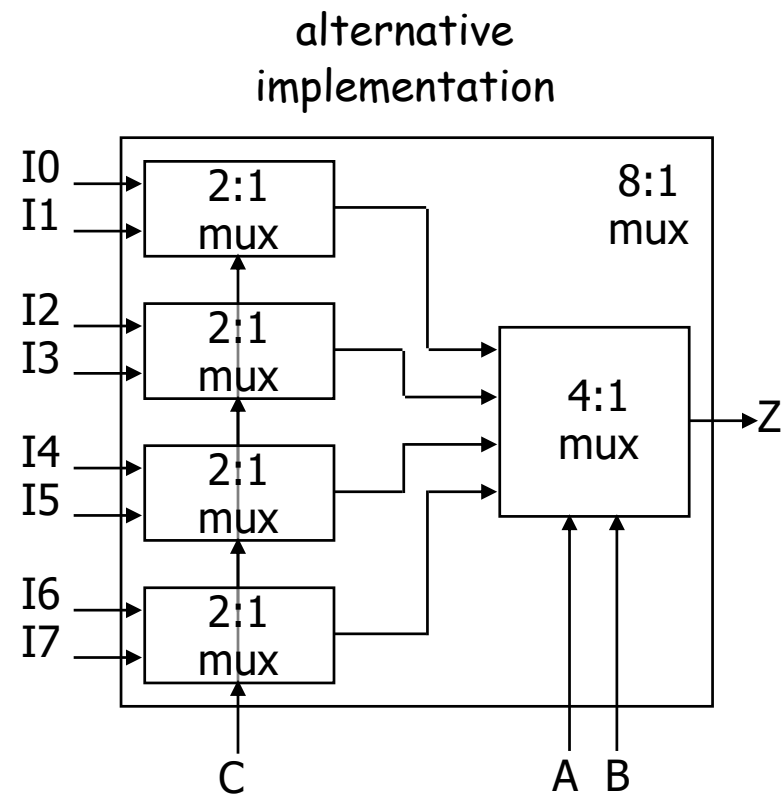control signal A chooses which of the upper or lower mux's output to gate to Z


 
# 多路选择器作为查找表 (Lookup Tables, LUTs)

- ❑  $2^n:1$  multiplexer implements any function of  $n$  variables
  - With the variables used as control inputs and
  - Data inputs tied to 0 or 1
  - In essence, a *lookup table*
- ❑ Example:
  - $F(A,B,C) = m_0 + m_2 + m_6 + m_7$   
 $= A'B'C' + A'BC' + ABC' + ABC$   
 $= A'B'(C') + A'B(C') + AB'(0) + AB(1)$




# 多路选择器作为查找表 (Lookup Tables, LUTs)

□  $2^{n-1}:1$  mux can implement any function of  $n$  variables


- With  $n-1$  variables used as control inputs and
- Data inputs tied to the last variable or its complement

□ Example:

 - $F(A,B,C) = m_0 + m_2 + m_6 + m_7$   
 $= A'B'C' + A'BC' + ABC' + ABC$   
 $= A'B'(C') + A'B(C') + AB'(0) + AB(1)$




A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

# 多路选择器作为查找表 (Lookup Tables, LUTs)


## Generalization

 

## Example: $F(A,B,C,D)$ implemented by an 8:1 MUX

				A	
				1	0
				0	1
C	1	0	1	1	0
	0	1	1	0	1
				D	
				1	0
				0	1
				B	

 choose A,B,C as control variables  
multiplexer implementation



# 解复器 / 译码器

## □ Decoders / demultiplexers: general concept

- Single data input, n control inputs,  $2^n$  outputs
- Control inputs (called "selects" (S)) represent binary index of output to which the input is connected
- Data input usually called "enable" (G)

1:2 Decoder:

$$O0 = G \bullet S'$$

$$O1 = G \bullet S$$

2:4 Decoder:

$$O0 = G \bullet S1' \bullet S0'$$

$$O1 = G \bullet S1' \bullet S0$$

$$O2 = G \bullet S1 \bullet S0'$$

$$O3 = G \bullet S1 \bullet S0$$

3:8 Decoder:

$$O0 = G \bullet S2' \bullet S1' \bullet S0'$$

$$O1 = G \bullet S2' \bullet S1' \bullet S0$$

$$O2 = G \bullet S2' \bullet S1 \bullet S0'$$

$$O3 = G \bullet S2' \bullet S1 \bullet S0$$

$$O4 = G \bullet S2 \bullet S1' \bullet S0'$$


$$O5 = G \bullet S2 \bullet S1' \bullet S0$$

$$O6 = G \bullet S2 \bullet S1 \bullet S0'$$

$$O7 = G \bullet S2 \bullet S1 \bullet S0$$
 
# 解复器作为通用逻辑

- $n:2^n$  decoder implements any function of  $n$  variables
  - With the variables used as control inputs
  - Enable inputs tied to 1 and
  - Appropriate min-terms summed to form the function




demultiplexer generates appropriate Min-term based on control signals (it "decodes" control signals)

# 解复器作为通用逻辑

$$\square F1 = A' B C' D + A' B' C D + A B C D$$

$$\square F2 = A B C' D' + A B C$$


$$\square F3 = (A' + B' + C' + D')$$

 

# 译码器级联

## □ 5:32 decoder


- 1x2:4 decoder
- 4x3:8 decoders

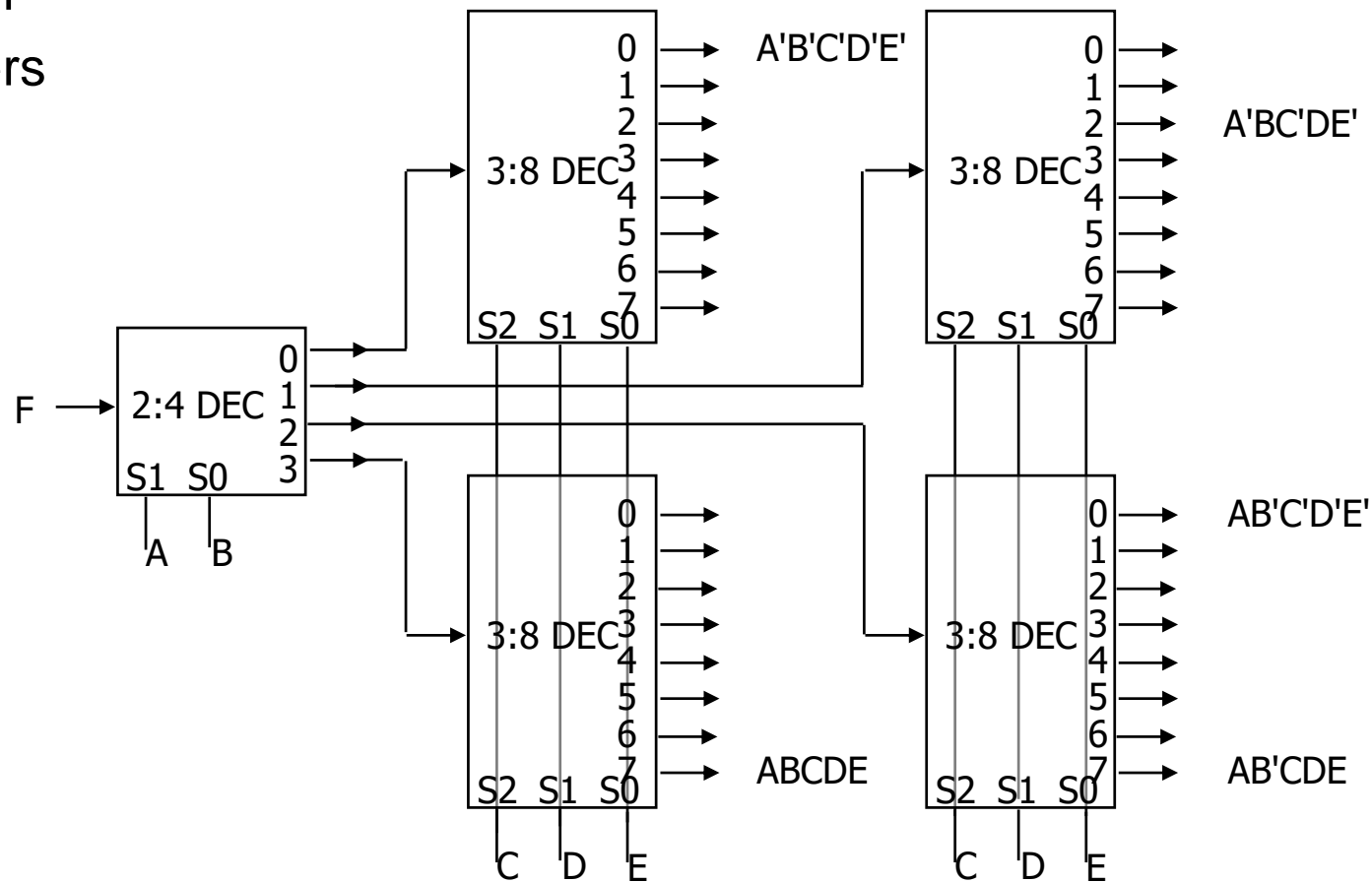


 
# 只读存储器 (ROM)

- ❑ Two dimensional array of 1s and 0s
  - Entry (row) is called a "word"
  - Width of row = word-size
  - Index is called an "address"
  - Address is input
  - Selected word is output



# ROM和组合逻辑

- Combinational logic implementation (two-level canonical form) using a ROM

$$F0 = A' B' C + A B' C' + A B' C$$


$$F1 = A' B' C + A' B C' + A B C$$

$$F2 = A' B' C' + A' B' C + A B' C'$$

$$F3 = A' B C + A B' C' + A B C'$$

A	B	C	F0	F1	F2	F3
0	0	0	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	1	0	0
0	1	1	0	0	0	1
1	0	0	1	0	1	1
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	1	0	1	0	0


truth table

 

block diagram
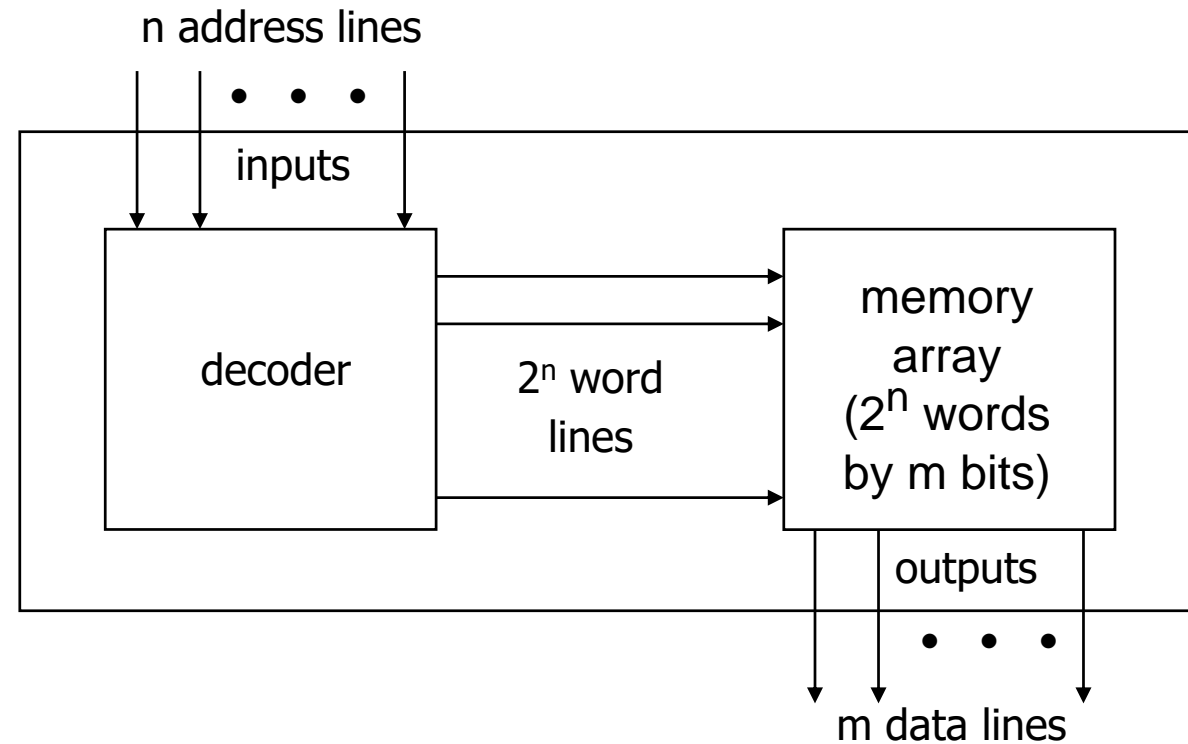
# ROM结构

- Similar to a PLA structure but with a fully decoded AND array
  - Completely flexible OR array (unlike PAL)



# ROM与 PLA对比


## □ ROM

- Design time is short (no need to minimize output functions)
- Most input combinations are needed (e.g., code converters)
- Little sharing of product terms among output functions
- Size doubles for each additional input
- Can't exploit don't cares
- Cheap (high-volume component)
- Can implement any function of  $n$  inputs
- Medium speed

## □ PLA

- Design tools are available for multi-output minimization
- There are relatively few unique min-term combinations
- Many min-terms are shared among the output functions
- Most complex in design, need more sophisticated tools
- Can implement any function up to a product term limit
- Slow (two programmable planes)


# 扩展字大小和存储容量

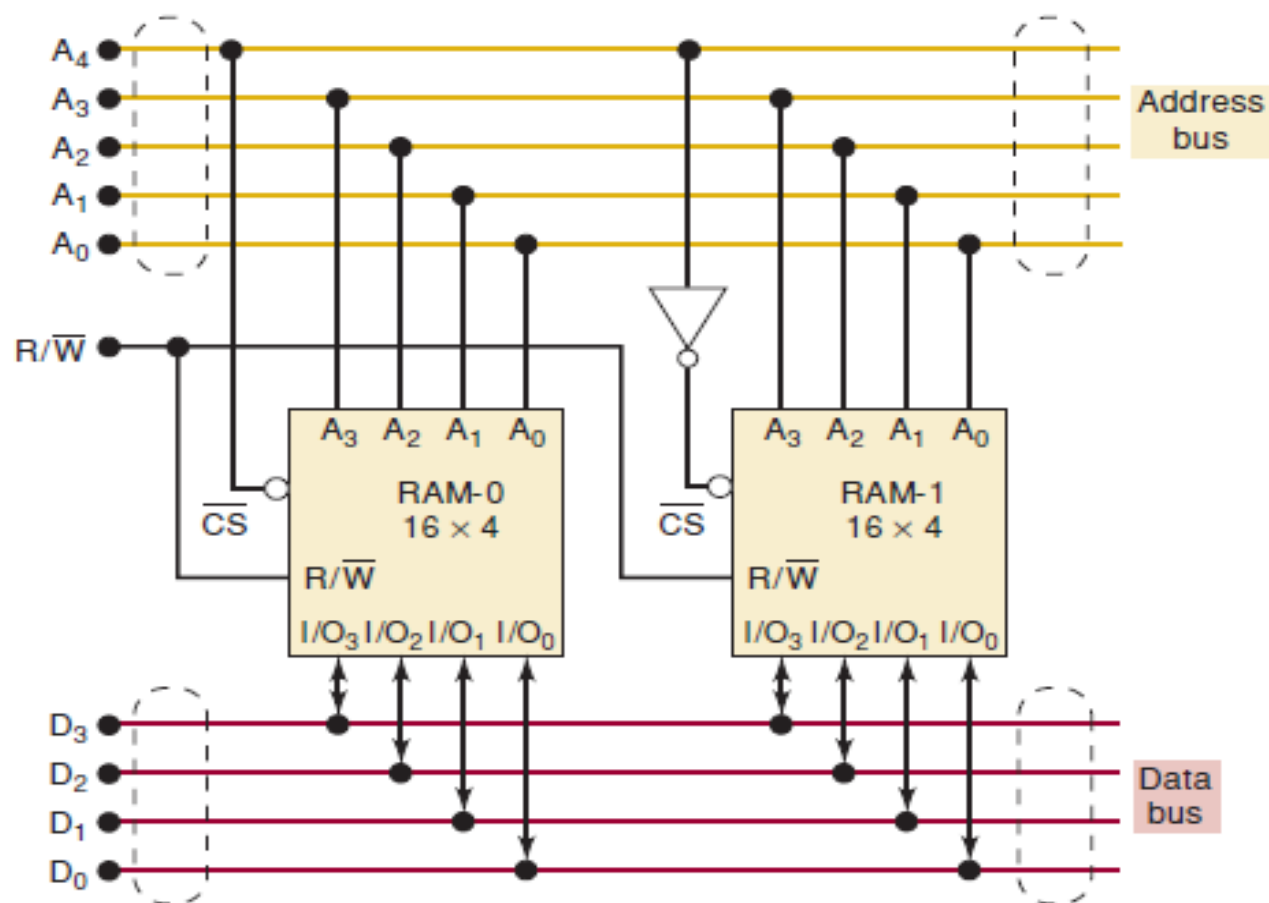

Address ranges: 00000 to 01111 – RAM-0  
10000 to 11111 – RAM-1

Total	00000 to 11111 – (32 words)
-------	-----------------------------

## 地址译码的系统例子

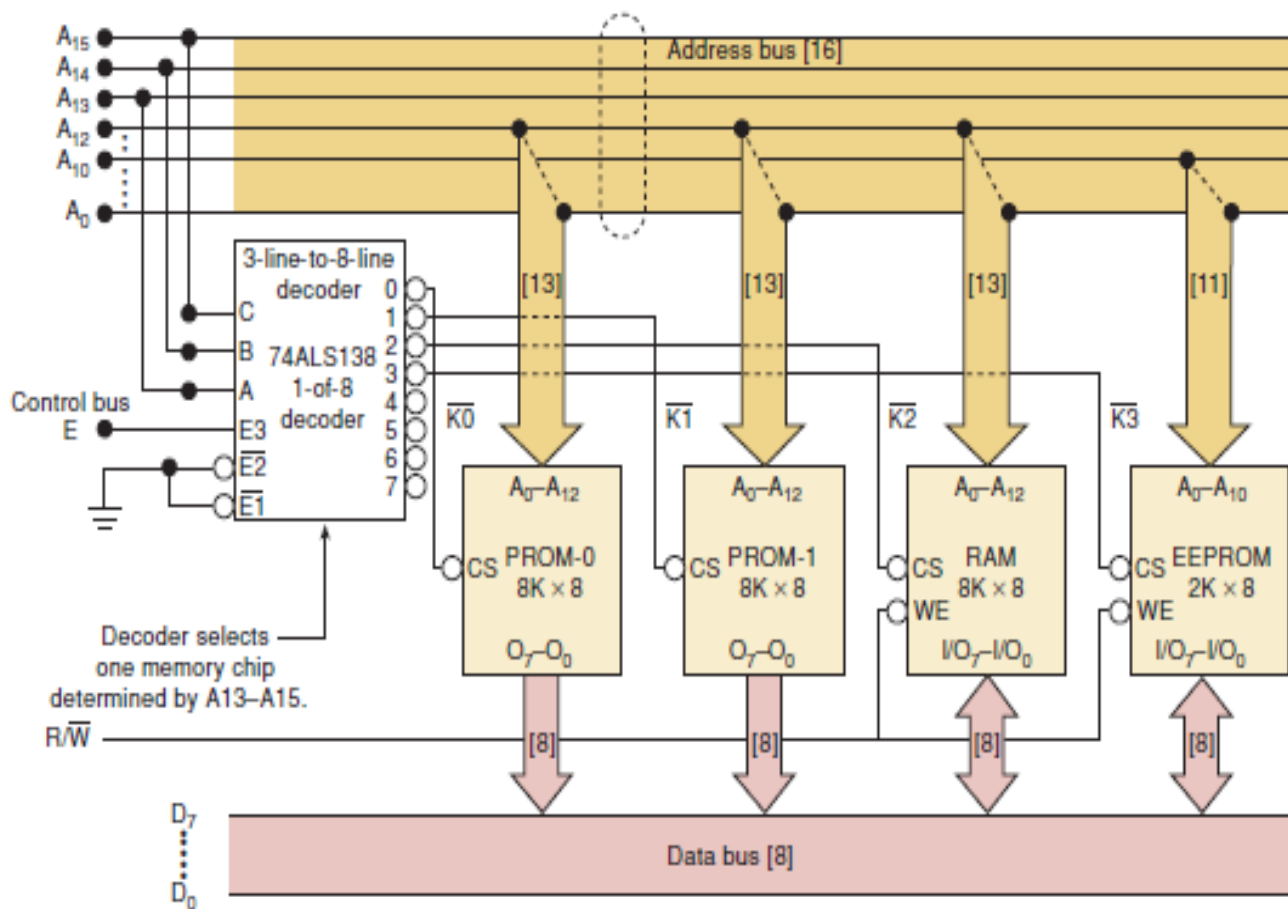

### Address ranges (hex)

0000 to 1FFF — PROM-0

## 2000 to 3FFF — PROM-1

4000 to 5FFF — RAM

## 6000 to 67FF — EEPROM

The diagram illustrates the memory layout of the device. It consists of two vertical columns representing memory addresses. The left column shows addresses from 0000 to 7FFF in increments of 1000. The right column shows addresses from 8000 to FFFF. A vertical arrow on the right side points downwards, labeled 'Available' at the top, indicating the range of available memory. The components are mapped as follows:

Address Range	Component
0000 - 1FFF	PROM-0
2000 - 3FFF	PROM-1
4000 - 5FFF	RAM
6000 - 67FF	EEPROM
6800 - 6FFF	EEPROM foldback
7000 - 77FF	EEPROM foldback
7800 - 7FFF	EEPROM foldback